

2025/FYUG/EVEN/SEM/
PHYDSC-252/045

FYUG Even Semester Exam., 2025

PHYSICS

(4th Semester)

Course No. : PHYDSC-252

(Electronics)

Full Marks : 70

Pass Marks : 28

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

UNIT—I

1. Answer any *two* of the following questions :

2×2=4

- (a) Define conductivity and mobility.
- (b) Define static and dynamic resistance of a *p-n* junction.
- (c) Explain the principle of LED.

J25/1268

(Turn Over)

(2)

2. Answer either [(a) & (b)] or [(c) & (d)] : 10
- (a) Explain in detail both forward and reverse bias characteristics of a $p-n$ junction diode with necessary diagram. Why is the current that flows during reverse bias condition across a $p-n$ junction diode called reverse saturation current? 4+1=5
- (b) Draw the circuit diagram of a full-wave rectifier. Find the expression of efficiency and ripple factor of a centre-tap full-wave rectifier. 1+4=5
- (c) Distinguish between Zener breakdown and Avalanche breakdown. 3
- (d) When do we consider a Zener diode to be in ON state and when do we consider to be in OFF state? Explain the working of a Zener diode as voltage regulator with necessary circuit diagram. 2+5=7

UNIT—II

3. Answer any two of the following questions : 2×2=4
- (a) Why is a transistor also called BJT?
- (b) Why is base of a transistor made extremely thin?
- (c) Define α . Show that it is less than unity.

J25/1268

(Continued)

(3)

4. Answer either [(a) & (b)] or [(c) & (d)] : 10
- (a) Draw the circuit diagram for plotting the input and output characteristics of a transistor in CE mode. Also explain the input and output characteristics of transistor in CE mode. 2+4=6
- (b) Explain the importance of Q -point. Also mention why it needs to be stabilized. 4
- (c) Explain the method of voltage divider biasing in detail with necessary circuit diagram and hence find the expression of stability factor. 6
- (d) In a CB configuration, the emitter current is 1 mA. If the emitter side is open, the collector current becomes $60 \mu\text{A}$. Find the value of total collector current I_c , if $\alpha = 0.9$. 4

UNIT—III

5. Answer any two of the following questions : 2×2=4
- (a) Why are h -parameters called hybrid parameters?
- (b) Explain the difference between virtual ground and real ground.
- (c) What is slew rate? What causes it?

J25/1268

(Turn Over)

(4)

6. Answer either [(a) & (b)] or [(c) & (d)] : 10

(a) Explain how $L-C$ oscillations are produced. Write down the condition for sustained oscillation. 3+1=4

(b) Explain the working of an $R-C$ phase shift oscillator in detail with necessary circuit diagram. Also mention the expression of its frequency of oscillation. 5+1=6

(c) For a $C-E$ transistor amplifier, find the expression of current gain, voltage gain, power gain using h -parameter. Also draw the h -parameter equivalent circuit for $C-E$ amplifier. 5+2=7

(d) Explain how OP-AMP can be used to work as an integrator. 3

UNIT—IV

7. Answer any two of the following as directed : 2×2=4

(a) Convert $(100)_{10}$ to binary.


(b) Illustrate the difference between SOP and CSOP with example.

J25/1268

(Continued)

(5)

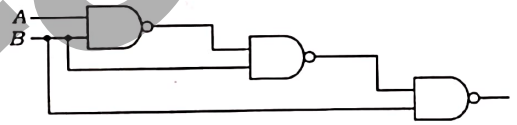(c) For which binary values of A and B , the output of the following circuit will be zero?



(i) $A = 0, B = 0$

(ii) $A = 0, B = 1$

(iii) $A = 1, B = 0$

(iv) $A = 1, B = 1$

(Choose the correct answer)

8. Answer either [(a) & (b)] or [(c) & (d)] : 10

(a) Prove the identity

$$AB + \overline{AC} + A\overline{B}C(AB + C) = 1 \quad 4$$

(b) Sketch a basic AND circuit with two diodes. Explain the operation of the circuit and hence find its truth table. 6

(c) For three variables A, B, C , list all the possible values of maxterms and minterms mentioning the symbol (designation) and representing terms corresponding each combination. 5

J25/1268

(Turn Over)

(6)

- (d) What do you mean by cell adjacency in the context of k -map? For the given truth table, draw the k -map and hence find the simplified expression : 1+4=5

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

UNIT—V

9. Answer any two of the following questions :

2×2=4

- (a) Add $(110011)_2$ and $(101101)_2$.
(b) Subtract $(1101)_2$ from $(1010)_2$ using 1's complement method.
(c) Mention two practical uses of demultiplexer.

10. Answer either [(a) & (b)] or [(c) & (d)] : 10

- (a) Explain the working of a full adder in detail with necessary circuit diagram and truth table. 4

J25/1268

(Continued)

(7)

- (b) Discuss the working of a J - K flip-flop with necessary logic circuit diagram and truth table. Also explain race around condition. 4+2=6
(c) What is the difference between arithmetic circuit and sequential circuit? Explain how one can realize full adder using half adder. 1+4=5
(d) Explain the working of a 4×1 MUX in detail with necessary circuit diagram and truth table. 5

J25—460/1268

2025/FYUG/EVEN/SEM/
PHYDSC-252/045